



COMBINATIONAL LOGIC

DECODER ENCODER

DIGITAL LOGIC DESIGN

Iqra Chaudhary (Lecturer CS dept. [NUML](#))


Binary Decoder

Binary decoder has n input lines and 2^n output lines

Only one output is a 1 for any given input

Extract “*Information*” from the code

Can be used to implement logic circuits

 


Decoders

★ Binary Decoder


- Binary to decimal representation
- Example: 2-bit Binary Number

Only *one* lamp will turn on

 


Decoders

★ 2-to-4 Line Decoder

 

I_1	I_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

$$Y_3 = I_1 I_0$$

$$Y_1 = \bar{I}_1 I_0$$

$$Y_2 = I_1 \bar{I}_0$$

$$Y_0 = \bar{I}_1 \bar{I}_0$$

Decoders

★ 3-to-8 Line Decoder

Truth Table:

x	y	z	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$$Y0 = x'y'z'$$

$$Y1 = x'y'z$$

$$Y2 = x'yz'$$

$$Y3 = x'yz$$

$$Y4 = xy'z'$$


$$Y5 = xy'z$$

$$Y6 = xyz'$$


$$Y7 = xyz$$

Decoders

★ 3-to-8 Line Decoder

 

Each output is a minterm

 


Decoders

★ “Enable” Control




E	I_1	I_0	Y_3	Y_2	Y_1	Y_0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

 

Decoders

- ★ Use enable input to make two 2 to 4 decoders to make 3 to 8 decoder
- ★ In this example, only one decoder can be active at a time.

$I_2 I_1 I_0$	$Y_7 Y_6 Y_5 Y_4$	$Y_3 Y_2 Y_1 Y_0$
0 0 0	0 0 0 0	0 0 0 1
0 0 1	0 0 0 0	0 0 1 0
0 1 0	0 0 0 0	0 1 0 0
0 1 1	0 0 0 0	1 0 0 0
1 0 0	0 0 0 1	0 0 0 0
1 0 1	0 0 1 0	0 0 0 0
1 1 0	0 1 0 0	0 0 0 0
1 1 1	1 0 0 0	0 0 0 0



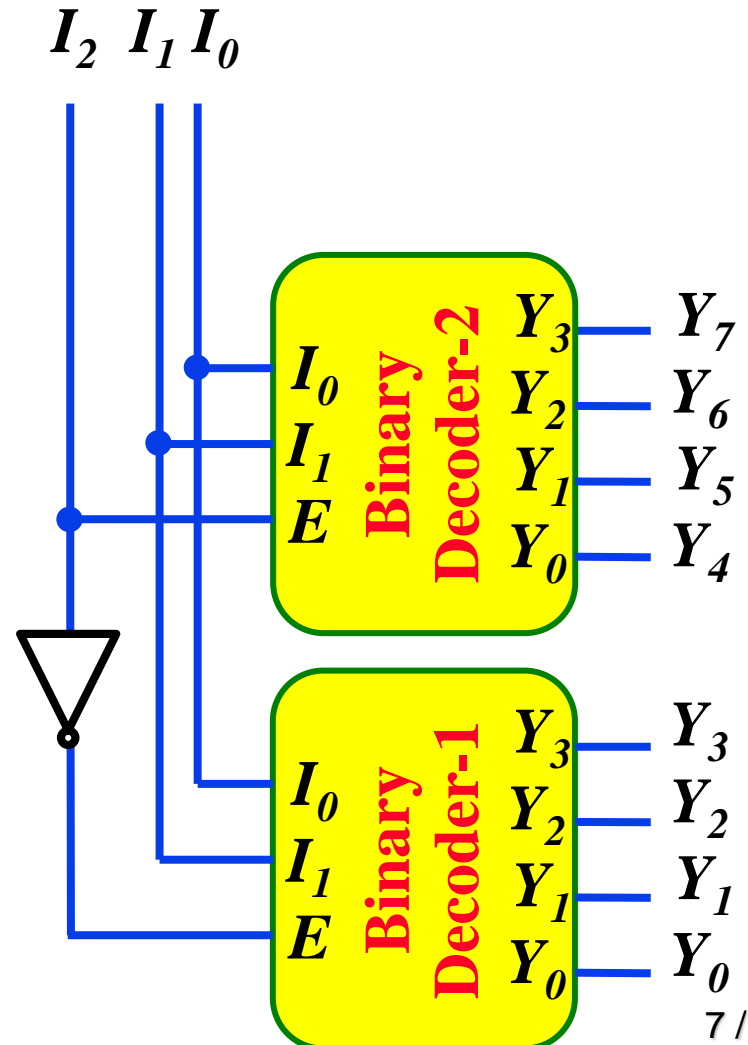


Decoders using NAND gate

★ Active-High/Active-Low(Note: use of NANDs only one 0 active!)

I_1	I_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

I_1	I_0	Y_3	Y_2	Y_1	Y_0
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	1	1	1

   

Implement combinational circuit by Using Decoders

- ★ Each output is a minterm
- ★ All minterms are produced
- ★ Sum the required minterms

x y z				
I_2	I_1	I_0	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Example: Full Adder

$$S(I_2, I_1, I_0) = \sum(1, 2, 4, 7) = \bar{I}_2\bar{I}_1I_0 + \bar{I}_2I_1\bar{I}_0 + I_2\bar{I}_1\bar{I}_0 + I_2I_1I_0$$

$$C(I_2, I_1, I_0) = \sum(3, 5, 6, 7) = \bar{I}_2I_1I_0 + I_2\bar{I}_1I_0 + I_2I_1\bar{I}_0 + I_2I_1I_0$$



$$S(x, y, z) = x'y'z + x'yz' + xy'z' + xyz$$

$$C(x, y, z) = x'yz + xy'z + xyz' + xyz$$


Implement full adder by Using Decoders

$$S(x, y, z) = \sum(1, 2, 4, 7) = xy'z' + x'yz' + x'y'z + xyz$$
  
$$C(x, y, z) = \sum(3, 5, 6, 7) = x'yz + xy'z + xyz' + xyz$$




BCD to Seven Segment Decoder

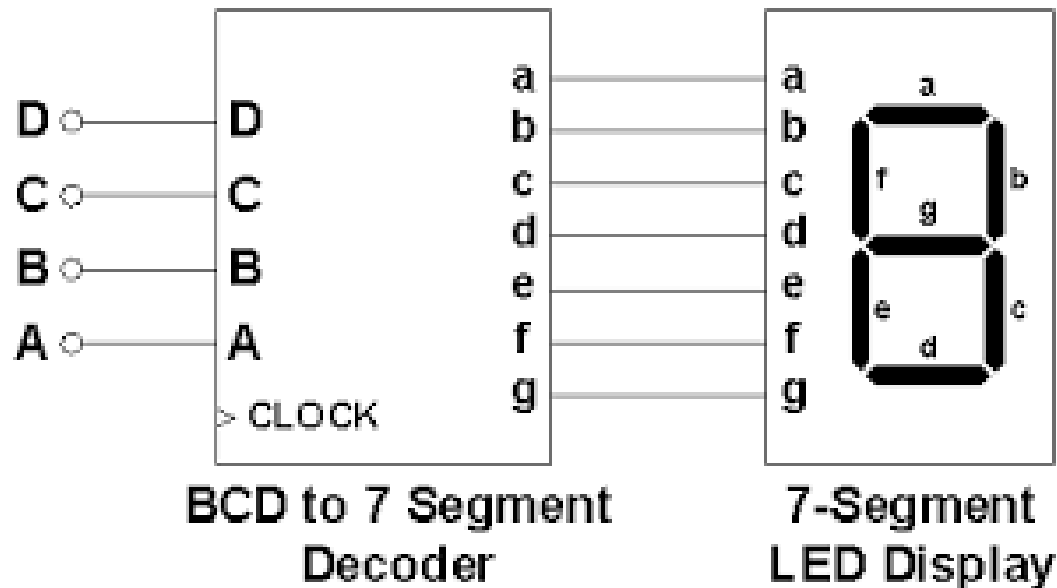

BCD to Seven Segment Decoder

- Decoder inputs data in BCD form and converts it to a seven segment output.
- The IC does the decoding that is involved in activating the appropriate segment outputs (a-g) that is required to represent the binary number that is inputted.
- There are 4 binary inputs to the Decoder and seven output segments (a-g).

BCD TO DECIMAL DECODER

 

For example if the BCD number 0100 (4) is input into the Decoder, the Decoder must activate outputs (b, c, f, g) because they form the digit 4.

Encoders

- ★ An encoder is a combinational logic circuit that essentially performs a “reverse” of decoder functions.
- ★ An encoder has 2^n number of input lines, only one of which input is activated at a given time and produces an n-bit output code , depending on which input is activated.
- ★ Put “*Information*” into code
- ★ An encoder accepts an active level on one of its inputs, representing digit, such as a decimal or octal digits, and converts it to a coded output such as BCD or binary. Encoders can also be devised to encode various symbols and alphabetic characters.

Binary Encoders



★ Octal-to-Binary Encoder (8-to-3)

I_7	I_6	I_5	I_4	I_3	I_2	I_1	I_0	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$Y_2 = I_7 + I_6 + I_5 + I_4$$

$$Y_1 = I_7 + I_6 + I_3 + I_2$$


$$Y_0 = I_7 + I_5 + I_3 + I_1$$

  


Binary Encoders(repeat)

At any one time, only one input line has a value of 1.

Inputs								Outputs		
I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7	y_2	y_1	y_0
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

 

Keyboard encoder

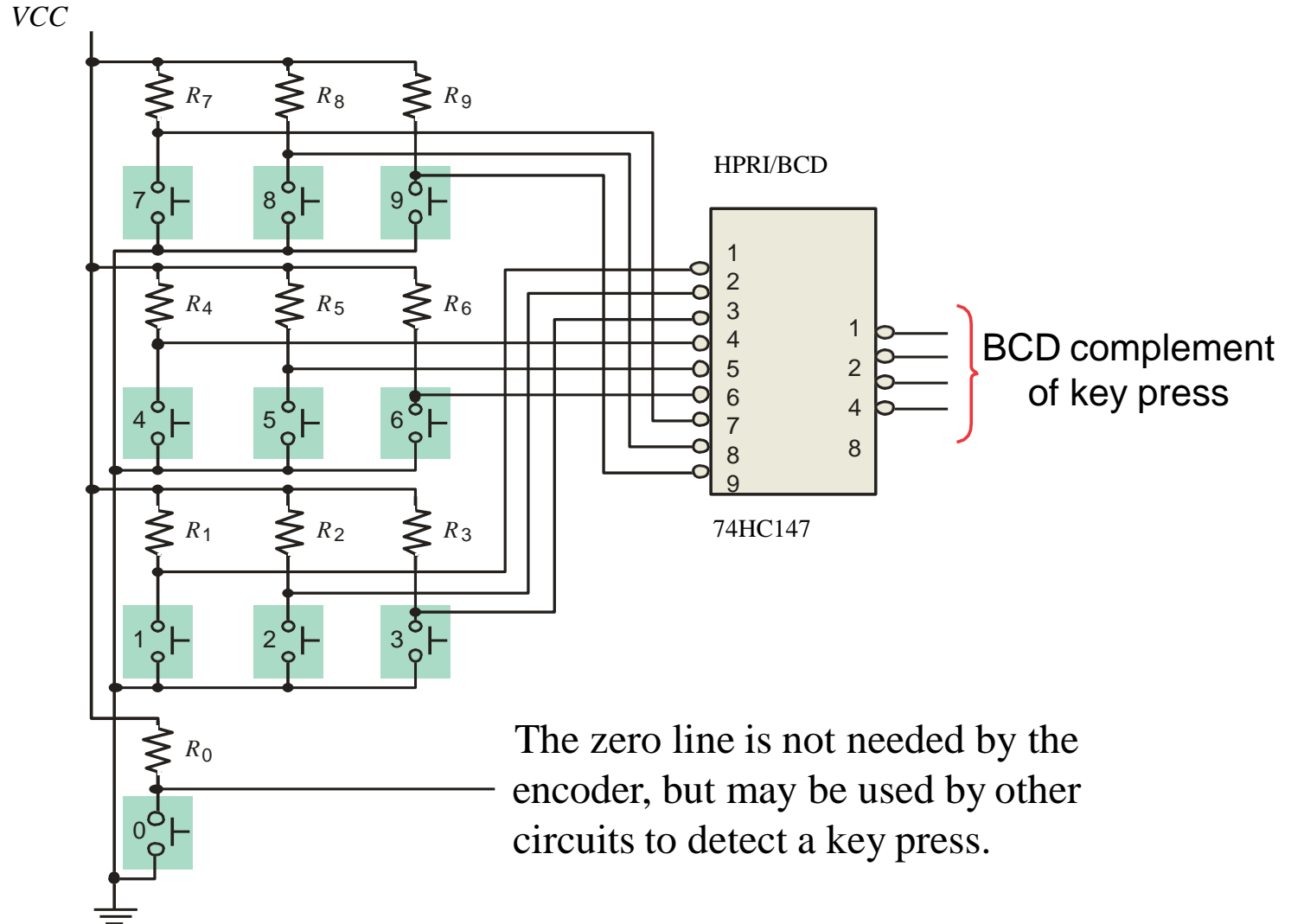

Encoder / Decoder Pairs

