



SEQUENTIAL LOGIC

SYNCHRONOUS SEQUENTIAL CIRCUITS
ASYNCHRONOUS SEQUENTIAL CIRCUITS
LATCHES(SR AND S'R' LATCH)
CONTROLLED LATCHES
D-LATCH

DIGITAL LOGIC DESIGN


Iqra Chaudhary (Lecturer CS dept. [NUML](#))

The story so far ...


- ★ Logical operations which respond to combinations of inputs to produce an output.
 - Call these combinational logic circuits.
- ✎ For example, can add two numbers. But:
 - No way of adding two numbers, then adding a third (a sequential operation);
 - No way of remembering or storing information after inputs have been removed.
- ✎ To handle this, we need sequential logic capable of storing intermediate (and final) results.

Sequential Circuits

★ Asynchronous

 


★ Synchronous

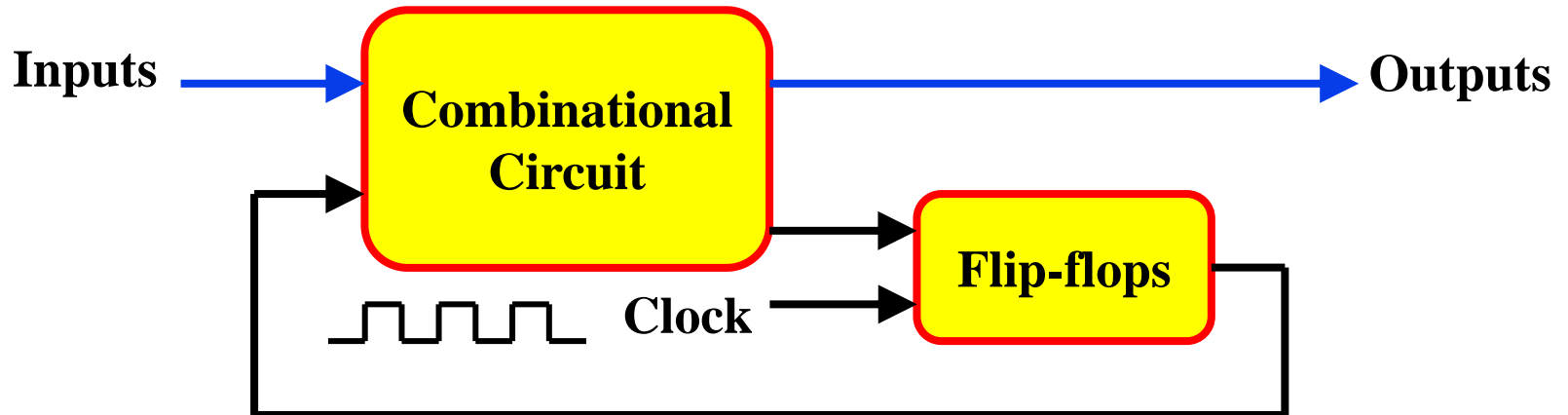

Latches (using Nor gate)

★ SR Latch

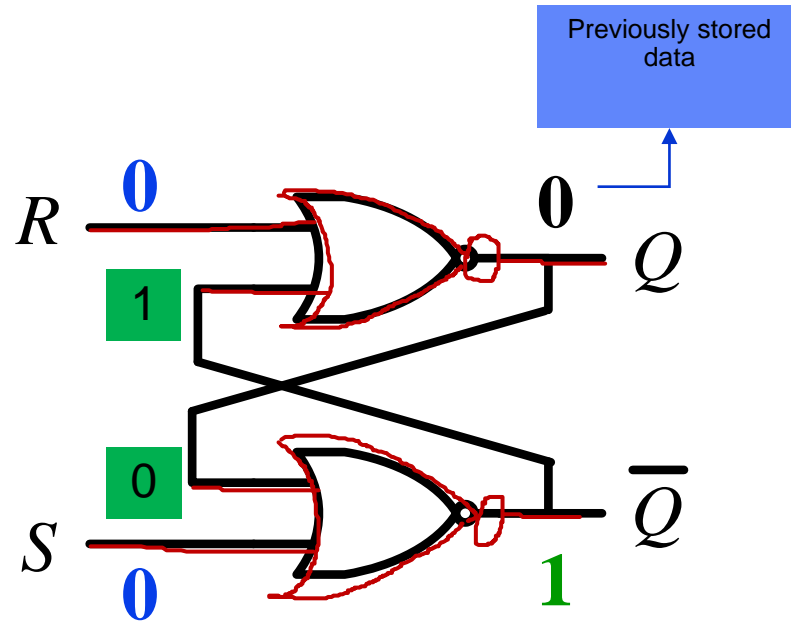

S	R	Q_0	Q	Q'
0	0	0	0	1


$$Q = Q_0$$

Input		Output
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

Initial Value

Latches

★ SR Latch

 

Input		Output
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

Previously stored value


Current value

S	R	Q_0	Q	Q'
0	0	0	0	1
0	0	1	1	0

$Q = Q_0$
 $Q = Q_0$

Latches

★ SR Latch

 

Input		Output
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

Previously stored value


Current value

S	R	Q_0	Q	Q'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1

} $Q = Q_0$
 $Q = 0$

Latches

★ SR Latch

 

Input		Output
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

Previously stored value

Current value

S	R	Q_0	Q	Q'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1

} $Q = Q_0$


$Q = 0$

$Q = 0$

Latches (Repeat)

★ SR Latch

Step 1:

 

Input		Output
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

Previously stored value

Current value

S	R	Q ₀	Q	Q'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1		


Q = Q₀

Q = 0

Latches (Repeat)

★ SR Latch

Step2:

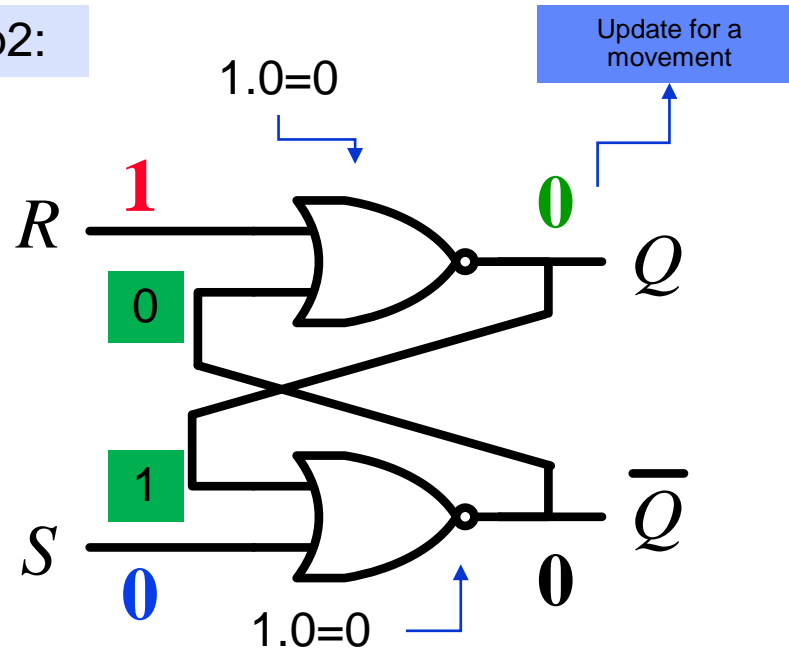


Input		Output
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

Previously stored value			Current value		
S	R	Q_0	Q	Q'	
0	0	0	0	1	} $Q = Q_0$
0	0	1	1	0	
0	1	0	0	1	} $Q = 0$
0	1	1			

Latches (Repeat)

★ SR Latch

Step 3:

 


Input		Output
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

Previously stored value			Current value		
S	R	Q_0	Q	Q'	
0	0	0	0	1	} $Q = Q_0$
0	0	1	1	0	
0	1	0	0	1	} $Q = 0$
0	1	1	0	1	

Latches

★ SR Latch

 


Input		Output
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

Previously stored value			Current value		
S	R	Q_0	Q	Q'	
0	0	0	0	1	} $Q = Q_0$
0	0	1	1	0	
0	1	0	0	1	} $Q = 0$
0	1	1	0	1	
1	0	0	1	0	$Q = 1$

Latches

★ SR Latch

 

Input		Output
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0


Previously stored value

Current value

S	R	Q_0	Q	Q'	
0	0	0	0	1	} $Q = Q_0$
0	0	1	1	0	
0	1	0	0	1	} $Q = 0$
0	1	1	0	1	
1	0	0	1	0	$Q = 1$
1	0	1	1	0	$Q = 1$

Latches

★ SR Latch

 

Input		Output
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0


Previously stored value

Current value

S	R	Q_0	Q	Q'	
0	0	0	0	1	} $Q = Q_0$
0	0	1	1	0	
0	1	0	0	1	} $Q = 0$
0	1	1	0	1	
1	0	0	1	0	} $Q = 1$
1	0	1	1	0	
1	1	0	0	0	$Q = Q'$

Latches

★ SR Latch

 

Input		Output
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0


Previously stored value

Current value

S	R	Q_0	Q	Q'	
0	0	0	0	1	} $Q = Q_0$
0	0	1	1	0	
0	1	0	0	1	} $Q = 0$
0	1	1	0	1	
1	0	0	1	0	} $Q = 1$
1	0	1	1	0	
1	1	0	0	0	$Q = Q'$
1	1	1	0	0	$Q = Q'$

Latches

★ SR Latch

 


S	R	Q
0	0	Q_0
0	1	0
1	0	1
1	1	$Q=Q'=0$

No change

Reset

Set

Invalid/undefine
state/forbidden state

 

S	R	Q
0	0	$Q=Q'=1$
0	1	1
1	0	0
1	1	Q_0

Invalid


Set

Reset

No change

Latches

★ SR Latch

 


S	R	Q
0	0	Q_0
0	1	0
1	0	1
1	1	$Q=Q'=0$

No change

Reset

Set

Invalid

 

S'	R'	Q
0	0	$Q=Q'=1$
0	1	1
1	0	0
1	1	Q_0

Invalid



Set

Reset

No change

Controlled Latches

★ SR Latch with Control Input

  

C	S	R	Q
0	x	x	Q_0
1	0	0	Q_0
1	0	1	0
1	1	0	1
1	1	1	$Q=Q'$

No change

No change



Reset

Set


Invalid

Controlled Latches

★ SR Latch with Control Input

  

The value of x can be 1 or 0



 


C	S	R	Q
0	x	x	Q_0

No change

Controlled Latches

★ SR Latch with Control Input

   



C	S	R	Q
0	x	x	Q_0
1	0	0	Q_0

No change

No change

Controlled Latches

★ SR Latch with Control Input

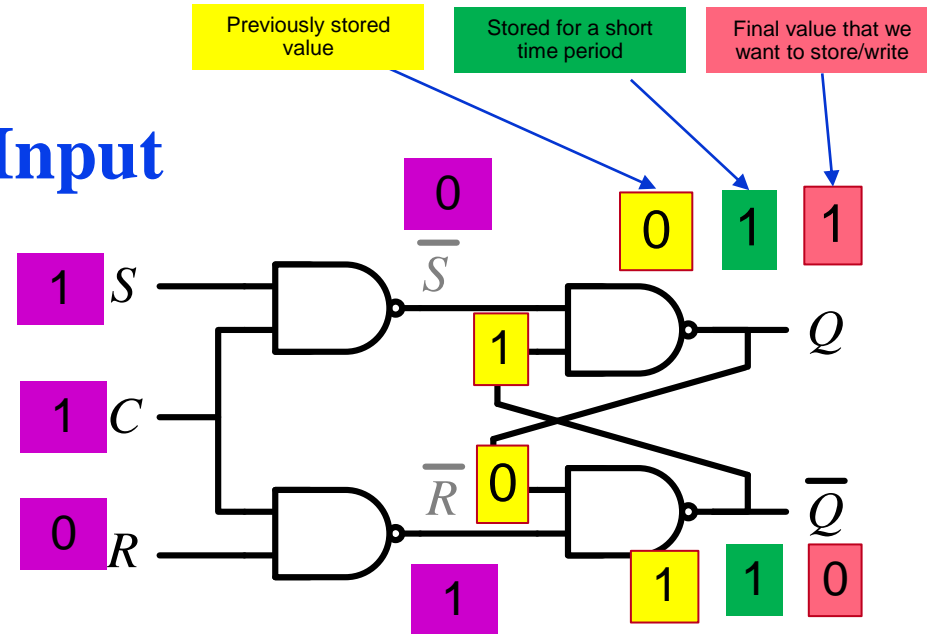 

C	S	R	Q
0	x	x	Q_0
1	0	0	Q_0
1	1	0	1



No change

No change

Set

Controlled Latches


★ SR Latch with Control Input

  

C	S	R	Q	
0	x	x	Q_0	No change
1	0	0	Q_0	No change
1	1	0	1	Set
1	1	1	$Q=Q'$	Invalid/Forbidden state
1	0	1	0	Reset

Controlled Latches

★ *D* Latch (*D* = *Data*)

 


<i>C</i>	<i>D</i>	<i>Q</i>
0	x	Q_0
1	0	0
1	1	1

No change

Reset


Set

Timing Diagram

 

Controlled Latches

★ *D* Latch (*D* = *Data*)

 


<i>C</i>	<i>D</i>	<i>Q</i>
0	x	Q_0
1	0	0
1	1	1

No change

Reset

Set

Timing Diagram

 

Output may change

Thanks