

Lecture Study Guideline

You need to follow three steps to study

Step 1: Watch the topic related video uploaded on LMS.

Step 2: Read the lecture notes attached.

Step 3: Read the topic from course book.

Topic: MOSFET Biasing

Step 1

Watch the topic related video uploaded on LMS.


Step 2

MOSFET Biasing

Three ways to bias a MOSFET.

- (1) zero bias.
- (2) Voltage-divider bias.
- (3) Drain feedback bias.

D - MOSFET bias (zero bias) :-

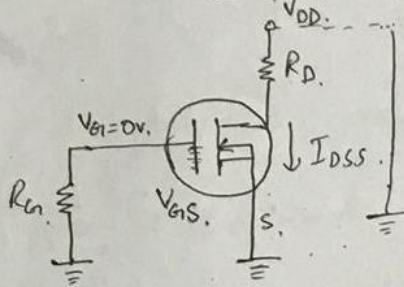


As we know that $V_{GS} = 0V$, $I_D = I_{DSS}$ (~~repeal~~ Repeal very few electrons from channel).


Apply KVL on above circuit.

$$V_{DS} = V_{DD} - I_{DSS} R_D$$

Purpose of R_{G1} is to accomodate an ac signal input by isolating it from ground.

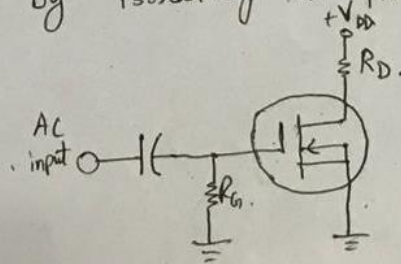

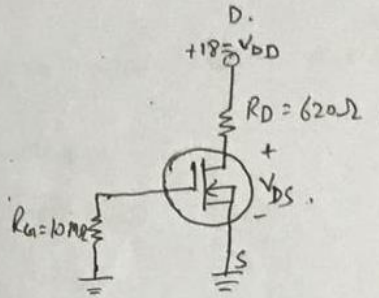Example 7-15. Determine the drain-to-source voltage in the circuit of fig. The MOSFET data sheet gives $V_{GS(off)} = -8V$ and $I_{DSS} = 12mA$.



As its zero bias circuit.

$$I_D = I_{DSS} = 12mA$$

drain to source voltage is.

$$V_{DS} = V_{DD} - I_D R_D.$$

$$V_{DS} = V_{DD} - I_{DSS} R_D.$$

$$V_{DS} = 18V - (12mA)(620\Omega)$$

$$V_{DS} = 10.6V.$$

class work when $V_{GS(off)} = -10V$ $I_{DSS} = 20mA$.

$$V_{DS} = ?$$

E-MOSFET bias :-


In E-MOSFET V_{GS} greater than the threshold value, $V_{GS(th)}$ so zero bias can not be used.

Two ways to bias an E-MOSFET.

→ Voltage divider.

→ Drain-feedback bias.

Voltage-divider:-

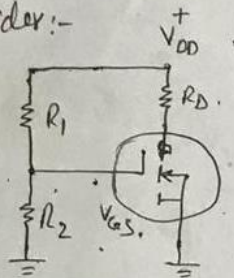


voltage divider bias.

$$V_{GS} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD}$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$\text{where } I_D = K (V_{GS} - V_{GS(th)})^2$$


Drain-Feedback bias :-

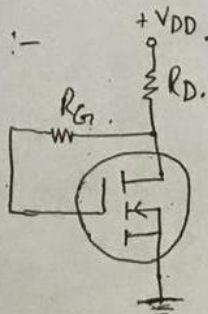

In drain feedback bias circuit, there is negligible gate current and therefore no voltage drop across

R_G . This makes $V_{GS} = V_{DS}$.

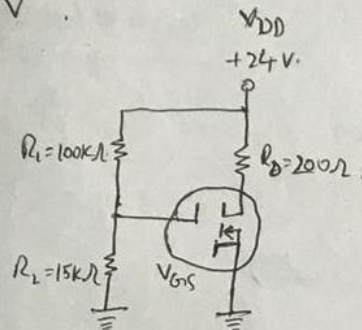Example 7-16:- Determine V_{GS} and V_{DS} for the E-MOSFET circuit in Fig. Assume this particular MOSFET has minimum values of $I_{D(on)} = 200 \text{ mA}$ at $V_{GS} = 4 \text{ V}$ and $V_{GS(th)} = 2 \text{ V}$.



$$V_{GS} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \left(\frac{15 \text{ k}\Omega}{115 \text{ k}\Omega} \right) 24 = 3.13 \text{ V}$$

$$\text{for } V_{DS} = V_{DD} - I_D R_D \quad \text{--- (1)}$$

we need to find I_D for $V_{GS} = 3.13 \text{ V}$.

$$I_D = K (V_{GS} - V_{GS(th)})^2 \quad \text{--- (2)}$$

Now first we will find K .

using assumption to find k .

2(b)

$$I_{D(on)} = 200 \text{ mA}$$

$$\text{at } V_{GS} = 4 \text{ V} \quad V_{GS(th)} = 2 \text{ V}$$

$$I_{D(on)} = k (V_{GS} - V_{GS(th)})^2$$

$$200 \text{ mA} = k (4 - 2)^2$$

$$k = \frac{200 \text{ mA}}{4 \text{ V}^2} = 50 \text{ mA/V}^2$$

$$\boxed{k = 50 \text{ mA/V}^2}$$

put this value of k in equ (2) to find I_D for $V_{GS} = 3.13 \text{ V}$.

$$I_D = 50 \text{ m} \left(\frac{3.13}{4} - 2 \right)^2$$

$$\boxed{I_D = 63.8 \text{ mA}}$$

using this value of I_D in equ (1)

$$V_{DS} = V_{DD} - I_D R_D$$

$$V_{DS} = 24 - (63.8 \text{ mA})(200 \Omega)$$

$$\boxed{V_{DS} = 11.2 \text{ V}}$$

$$\boxed{V_{GS} = 3.13 \text{ V}}$$

Step3: Read topic 7.5, 7.6 from text book (Thomas L Floyd 7th edition)