

Experiment#4

Title:-

Application of logic gates “Implementation of distributive law”

Objective:-

- **Distributive law**
 - $A(B + C) = AB + AC$
 - $(A + B)(C + D) = AC + AD + BC + BD$

Parts required:-


- IC Type 7408 Quadruple 2-input AND gates
- IC Type 7432 Quadruple 2-input OR gates

Equipment required:-

- Trainer/ proto board
- Wire cutter
- Patch Cord
- Voltmeter

Theory:-

Distributive law

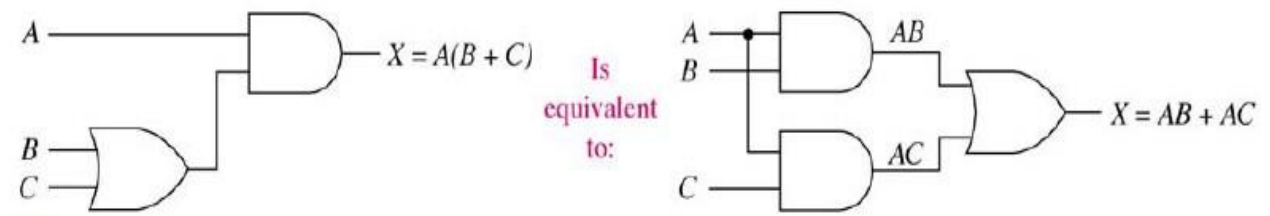

Procedure:-

- (a) Place the IC of required on the bread board. Be sure that it is seated firmly, straddling the notch in the socket, and that none of the pins are bent
- (b) connect $V_{cc}=5V$ to pin 14 and Ground to pin 7
- (c) Pin lay out of the IC is given in Annex connect one of gates. Connect inputs(pin1&2)to SW1 and SW2 and output to the LED
- (d) Switch ON the circuit and complete following truth tables for both cases for distributive law

$$A (B+C) = AB+AC$$

A	B	C	B+C	A(B+C)	AB	AC	AB+AC
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

Question:- Draw the logic circuit diagrams and describe the connections.