

# Lecture Study Guideline

## **You need to follow three steps to study**

Step 1: Watch the topic related video uploaded on LMS.

Step 2: Read the lecture notes attached.

Step 3: Read the topic from course book.

## **Topic: collector characteristic curve of transistor**



### **Step 1**

Watch the topic related video uploaded on LMS.
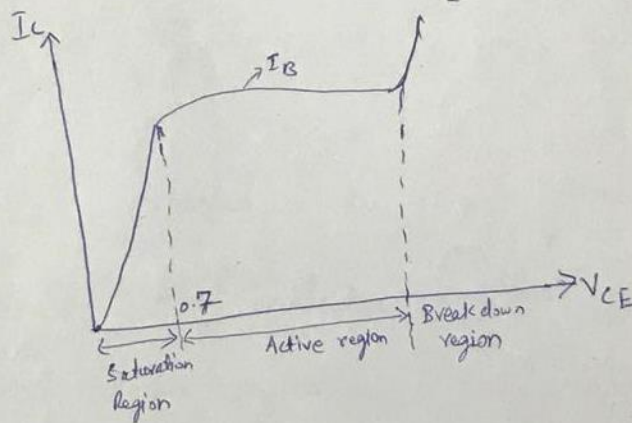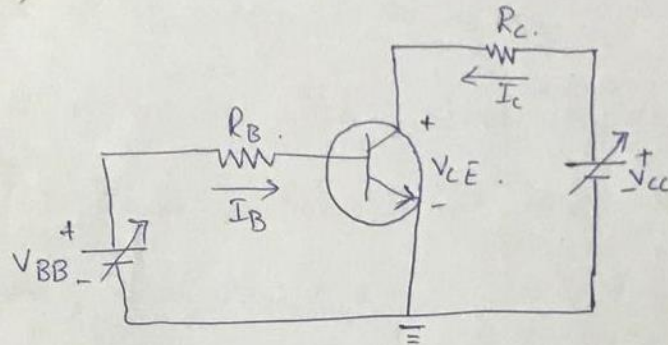
## Step 2

Collector characteristic Curves :-

These curves show how the collector current  $I_C$  varies with collector to emitter voltage ( $V_{CE}$ ) for specified values of base current ( $I_B$ ).



- i)  $V_{BB}$  = certain value  $I_B$  = small  $I_B$  produces  $V_{CE} = \text{zero}$   
Base emitter junction (F.B), Base collector junction (F.B)  
Transistor is in saturation region.  
 $V_{CE}$  is very low.  $I_C$  = zero initially and increases rapidly in saturation region.

(ii)  $V_{CC}$  = increased.  $V_{CE}$  increases gradually.

Base emitter junction (F.B), Base collector junction become (R.B) after 0.7V of  $V_{CC}$ .

This region is called active <sup>or linear</sup> region. As

Base collector junction become (R.B) then  $I_C$  become nearly constant.

$$I_C = \beta_{DC} I_B.$$


(iii)  $V_{CE}$  increased, so high that Reverse biased base collector junction goes into break down region.

Transistor should not be operated into break down region.  $I_C$  become so high.

Cutoff region :-

When  $I_B = 0$  transistor is in cutoff region.

$$V_{CE} = V_{CC}$$

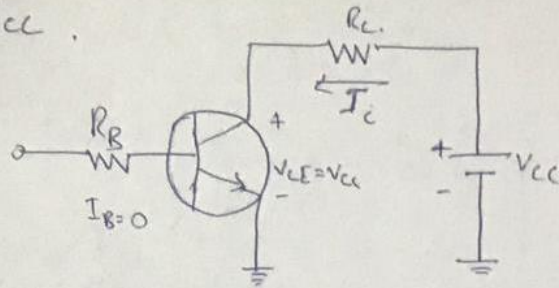


$I_C$  is very small

Both base-emitter and base collector junctions are reverse biased.

	Base emitter Junction	Base collector Junction
Saturation Region	Forward biased $V_{BE}$ has some value.	Forward biased $V_{CE} < 0.7$ .
Active Region	Forward biased $V_{BE}$ has some value.	Reverse biased $V_{CE} > 0.7V$ .
Cutoff	Reverse biased $V_{BE} = 0$ .	Reverse biased $V_{CE}$ .





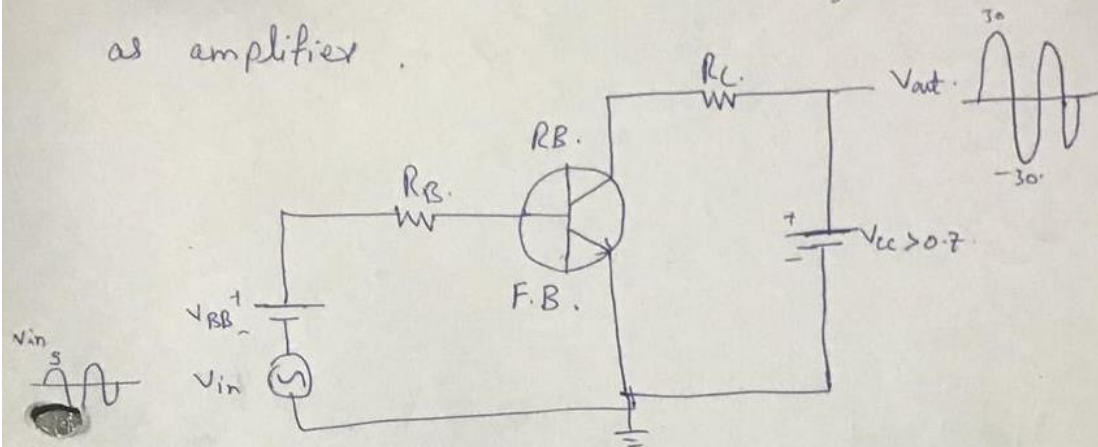Transistor is biased into active region to work as amplifier.



Transistor is biased into cut off <sup>or saturation.</sup> region to

work as switch.

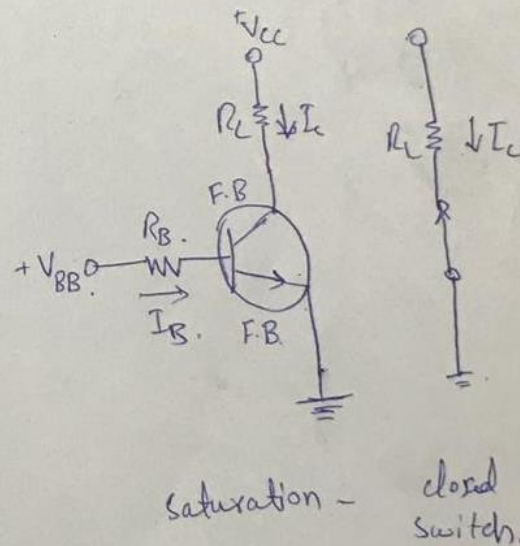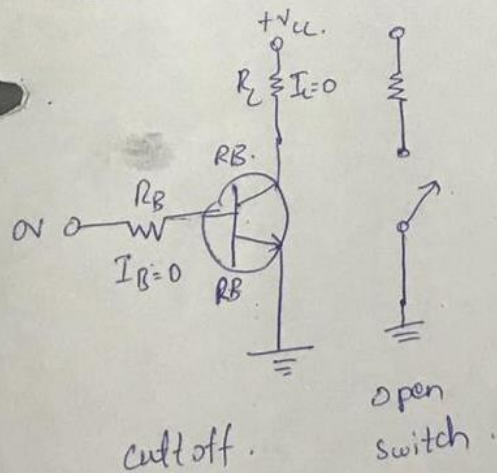

Step3: Read topic 4.3 from text book (Thomas L Floyd 7<sup>th</sup> edition)


## **Topic: Q-point of transistor**


### **Step 1**

Watch the topic related video uploaded on LMS.


## Step 2
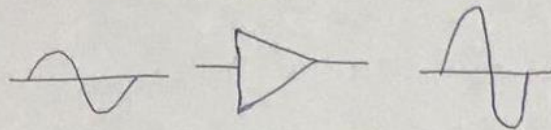
### Transistor bias circuits. (CH #5)


Amplifier symbol   
Transistor as amplifier:



(a) Linear operation.

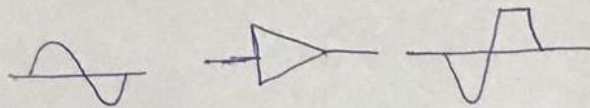

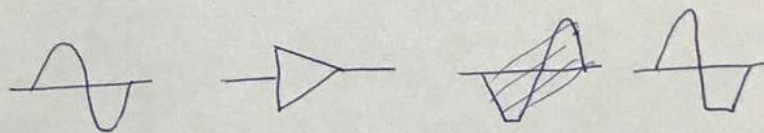(b) cutoff region (output voltage clipped)





(c) Saturation region (output voltage clipped)

Case (b) and (c) is because of improper biasing.

To overcome this problem we chose Q point.



# Graphical Analysis:-

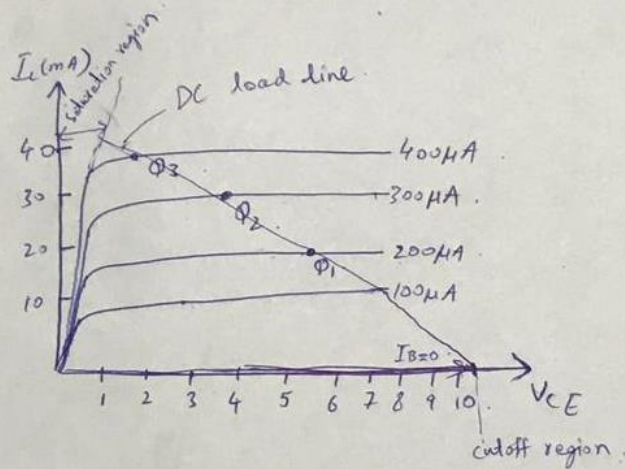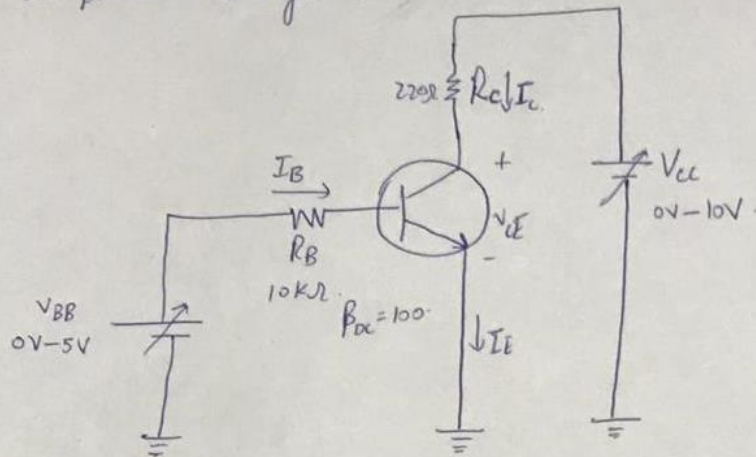

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$I_B = 200\mu A \quad I_C = \beta_{DC} I_B = 100 \times 200\mu A = 20mA$$

$$V_{CE} = V_{CC} - I_C R_C = 10 - (20mA)(220) = 10 - 4.4$$

$$Q_1 \quad \boxed{V_{CE} = 5.6V} \quad \boxed{I_C = 20mA}$$

$$I_B = 300\mu A \quad I_C = 30mA \quad V_{CE} = 3.4V, \quad Q_2$$

$$I_B = 400\mu A \quad I_C = 40mA \quad V_{CE} = 1.2V, \quad Q_3$$

As  $I_B$  increase,  $I_C$  increase,  $V_{CE}$  decrease  
 $I_B$  decrease,  $I_C$  decrease,  $V_{CE}$  increase.

By changing  $V_{BB}$  we will change  $I_B$  and our  $Q$  point will move on dc load line.


Linear operation :-

we will chose  $Q$  point between saturation region and cutoff region on the DC load line.

Example :

Determine the  $Q$  point of the circuit?

$\beta_{DC} = 200$

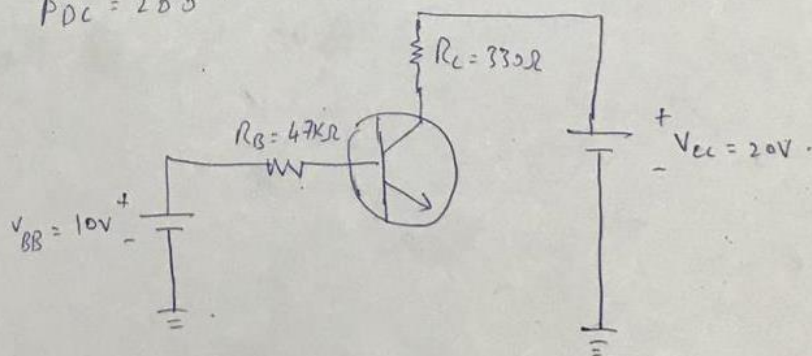

Linear region:

1(c)

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{10V - 0.7V}{47k\Omega} = 198\mu A$$

$$I_C = \beta_{DC} I_B = (200)(198\mu A) = 39.6mA$$

$$V_{CE} = V_{CC} - I_C R_C = 20V - 13.07V = 6.93V$$

Q-point  $I_C = 39.6mA$  at  $V_{CE} = 6.93V$

cutoff:


$$I_B = 0, I_{C(cutoff)} = 0, I_C = \beta_{DC} I_B$$

$$V_{CE} = V_{CC} \text{ (ideal)}$$

saturation region:

$$V_{CE} = V_{CC} - I_{C(sat)} R_C, V_{CE} = 0 \text{ (ideal)}$$
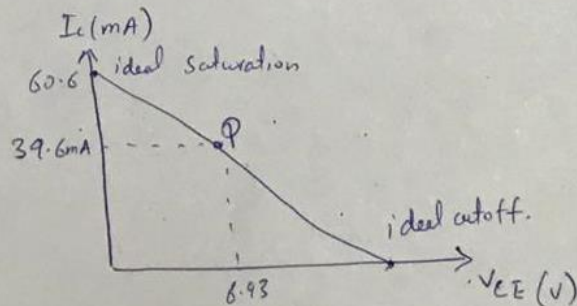
$$I_C = \frac{V_{CC}}{R_C} = \frac{20V}{330} = 60.6mA$$



Step3: Read topic 5.1 from text book (Thomas L Floyd 7<sup>th</sup> edition)