

# Diode Applications

Property of diode :-

It conducts current in one direction while blocking in the other direction


Diodes are used in

(a) DC power supply

It converts AC into constant DC voltage


This DC voltage is used into television, CD players and most laboratory equipment.

Block diagram of DC power supply :-

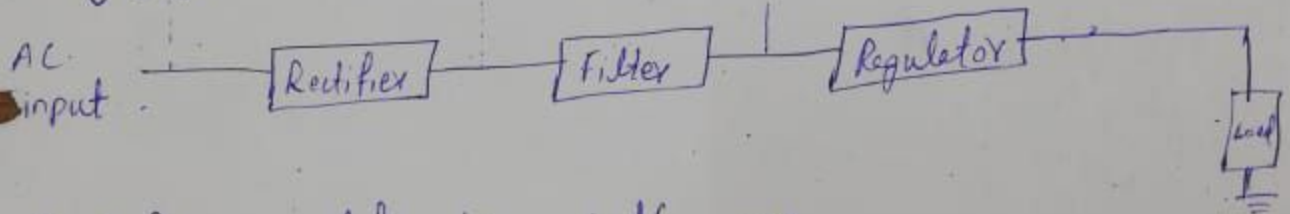


Rectifier could be half wave  
Full wave

Half wave rectifier :-

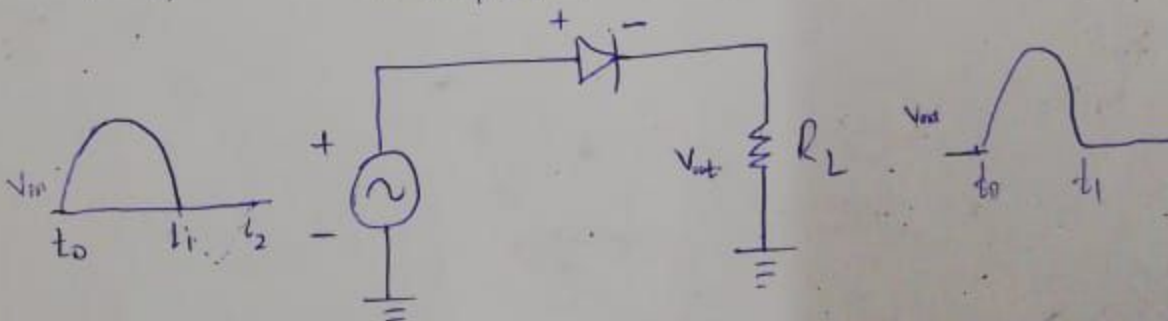


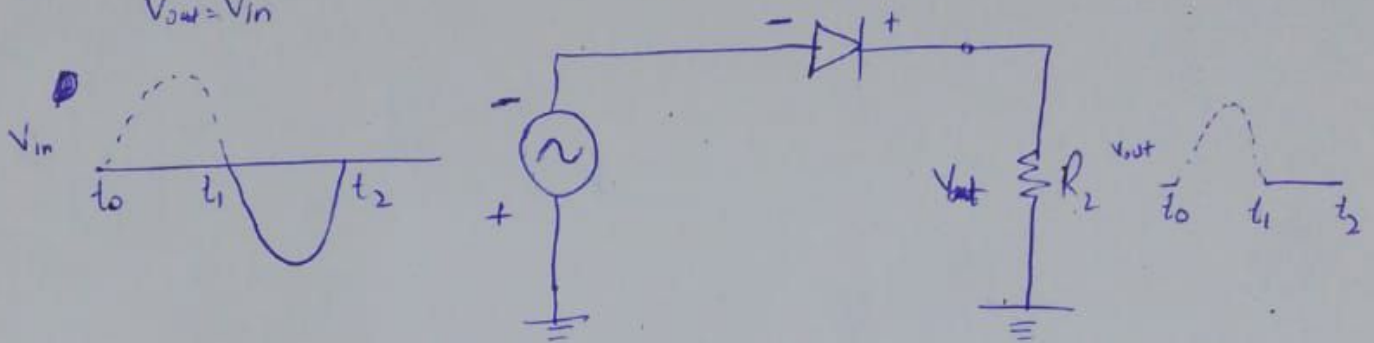Considering the ideal model of diode. when the input is positive half cycle diode behave as forward bias and conducts current through the load resistor  $R_L$ .  
 $V_{out} = V_{in}$




During the negative half cycle diode act as reverse bias and no current will flow through  $R_L$ . And voltage across  $R_L$  is zero. so  $V_{out} = 0$  during negative half cycle.

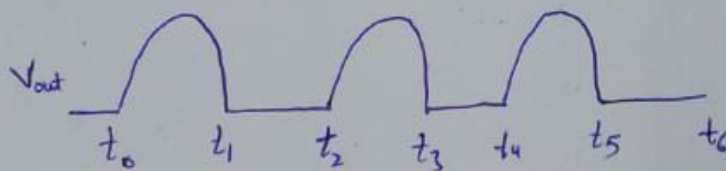
Complete output voltage for HW rectifiers. for three cycles.



Effect of the barrier potential in case of practical diode.

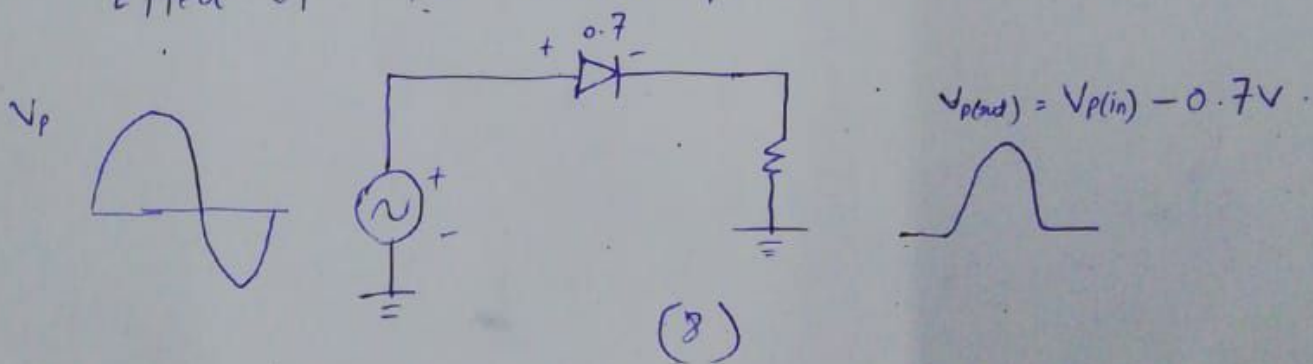


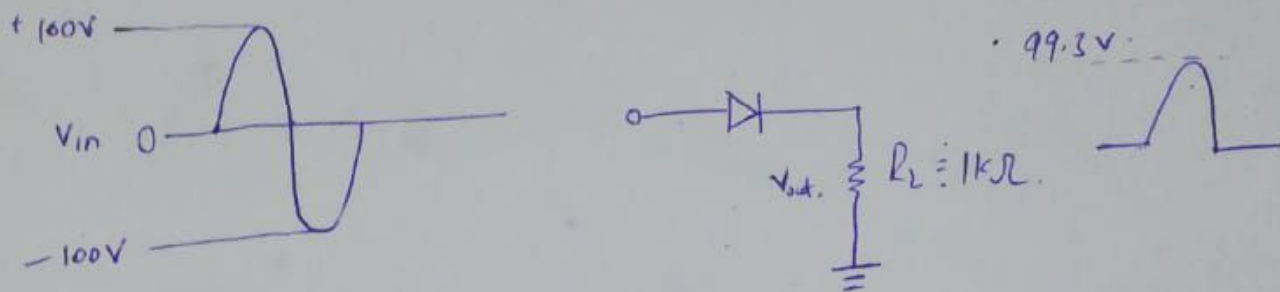Example 2-2 :- Draw the output voltage of <sup>the</sup> ~~each~~ rectifier for the indicated input voltages?  
consider practical diode




Full wave Rectifiers :-

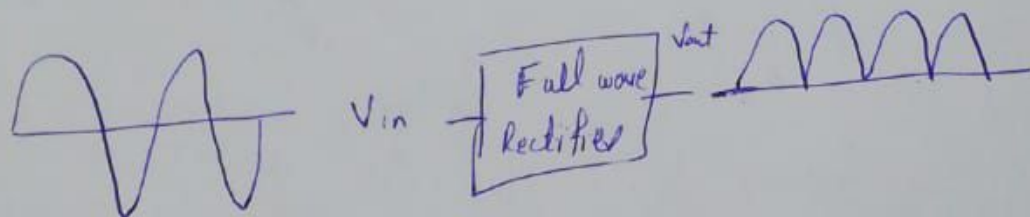A full wave rectifier allows current through the whole cycle.



Bridge Full-wave Rectifier :-


It uses four diodes

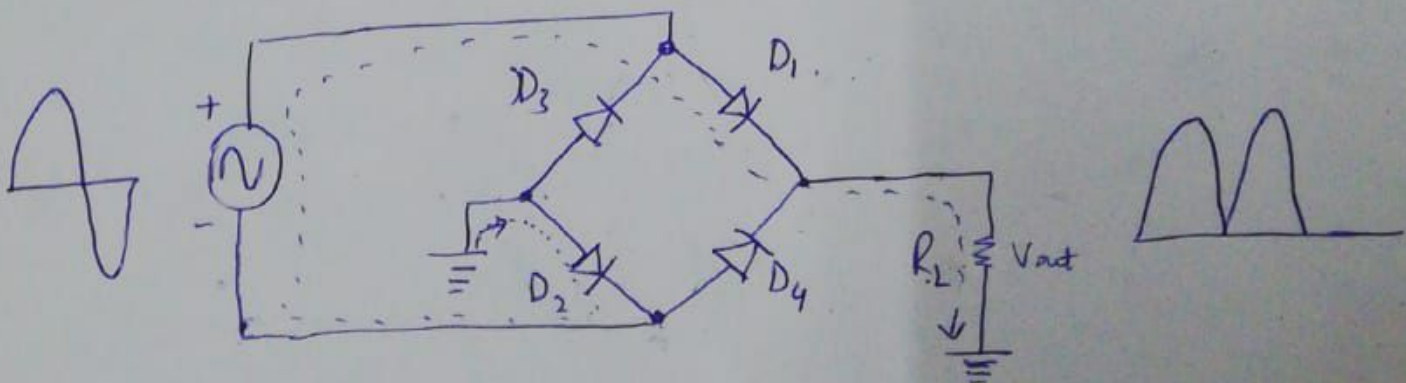




During positive cycle  $D_1$  &  $D_2$  act as forward bias and conduct current.  $D_3$  &  $D_4$  act as reverse bias.

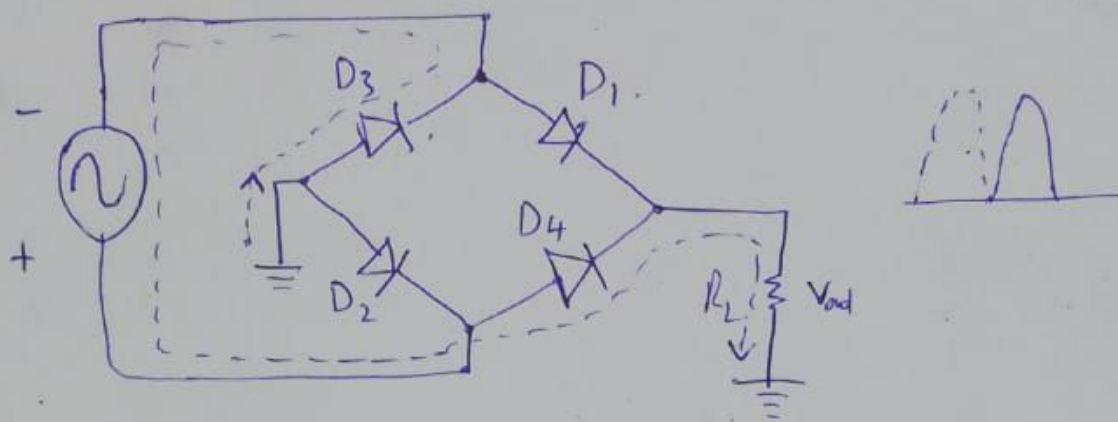
During negative cycle  $D_3$  &  $D_4$  act as forward bias and conduct current in the same direction as it was during positive half cycle.




Practical model output of full wave Rectifier.

$$V_{out} = V_{in} - 1.4$$


Power Supply filters and Regulators :-

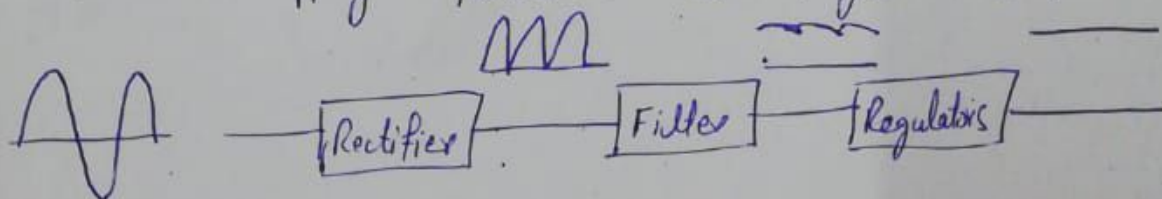

Filters :- Capacitor input filter,

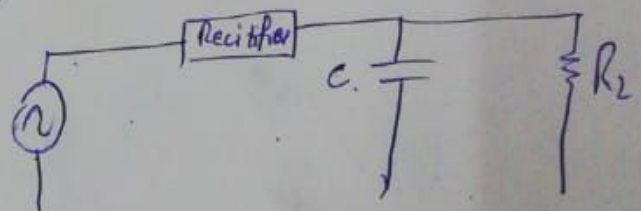

It reduces ripples  
 $< 10\%$


# Diode Limiting and damping circuits :-

Diode limiter circuits are used to clip off some portion of signal.
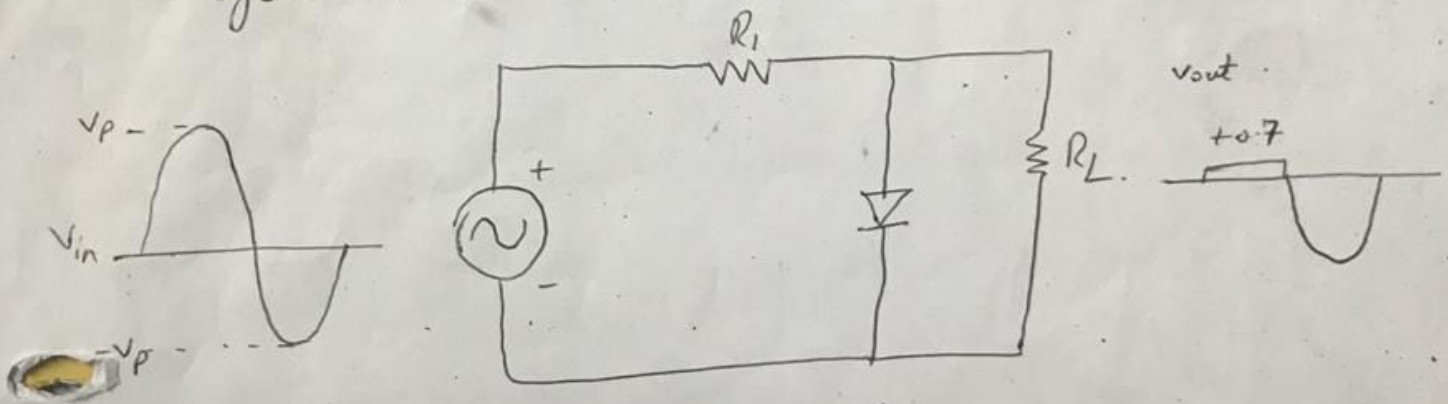
## Diode Limiters :-

clips Positive half cycle :-

Diode become forward biased for +ve half cycle after 0.7V (silicon). For -ve half cycle diode become reverse biased.




$$V_{out} = V_{in} \left( \frac{R_L}{R_1 + R_L} \right)$$


$$R_1 \ll R_L \quad V_{out} = V_{in}$$

clips negative half cycle :-

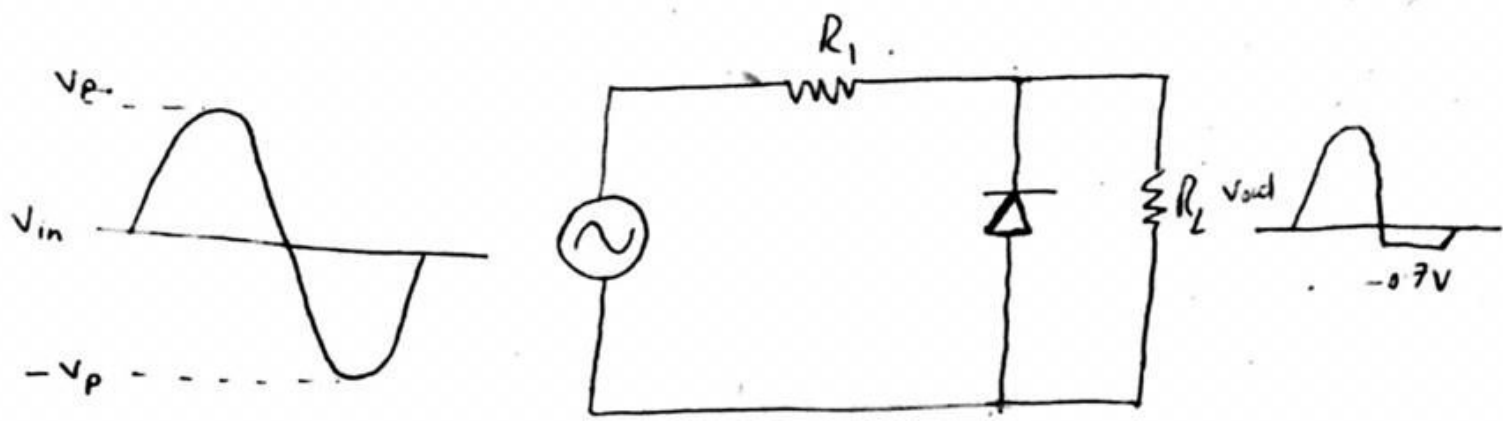Diode become reverse biased for +ve half cycle. For -ve half cycle diode become forward biased after -0.7V.




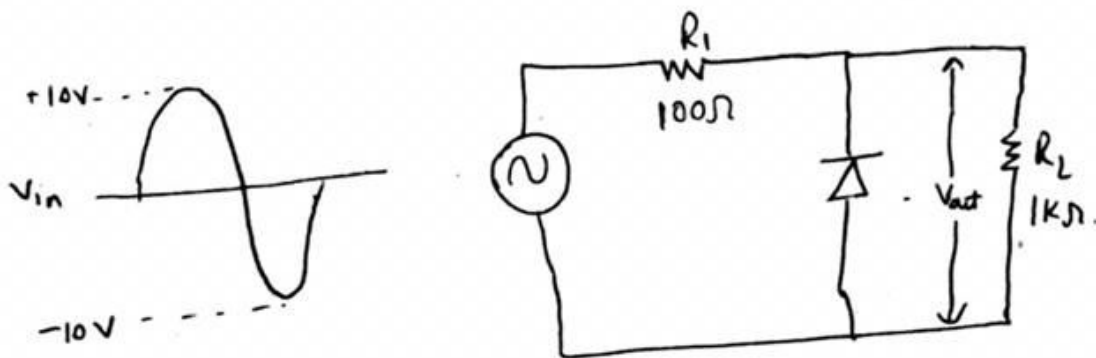Example. What would be output against  $R_L$ ?



Diode is forward biased and conducts when the input voltage goes below  $-0.7V$ .

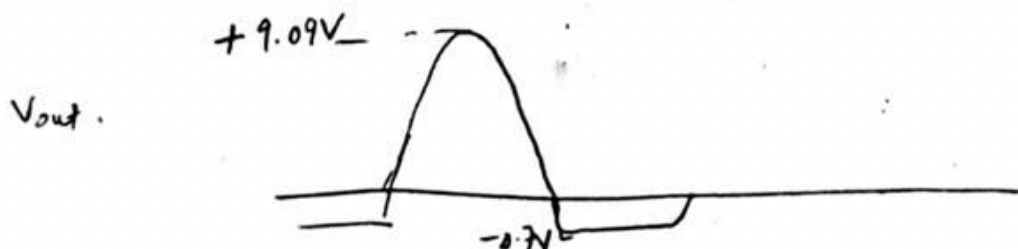
$$V_{p(out)} = \left( \frac{R_L}{R_1 + R_L} \right) \cdot V_{p(in)} = \left( \frac{1k\Omega}{100\Omega + 1k\Omega} \right) \times 10 = 9.09V$$






## Biased Limiters :-


### Positive limiter .

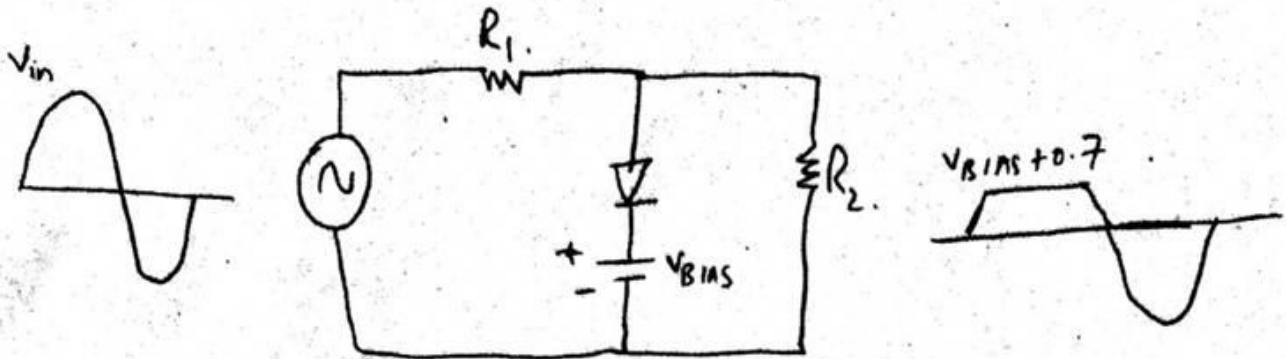

### Negative limiter .

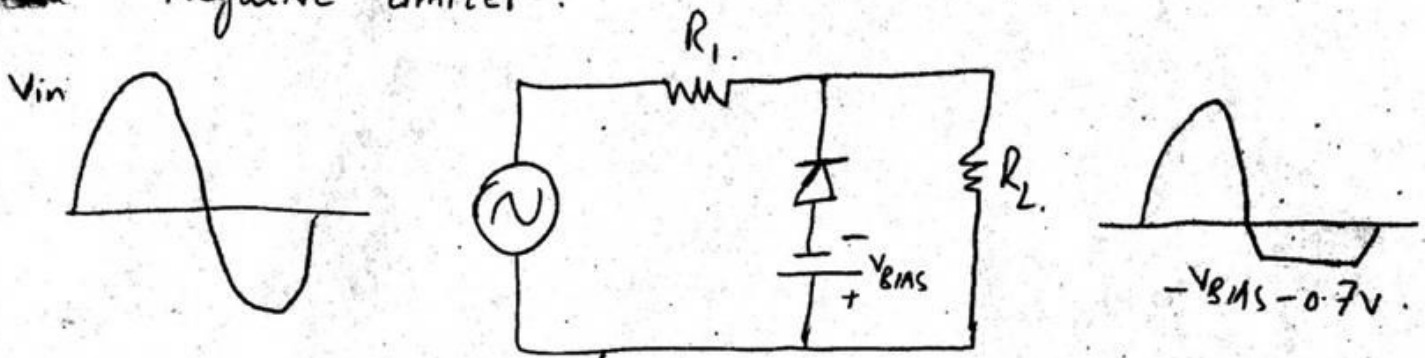


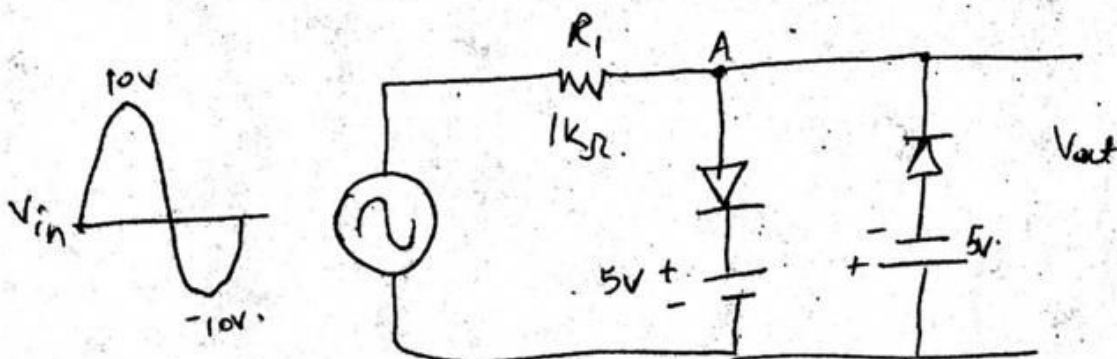Example : Circuit combining a positive limiter with a negative limiter .




Voltage at point A reaches  $+5.7V$ .  
 diode  $D_1$  conducts and limits the <sup>pos</sup> waveform.

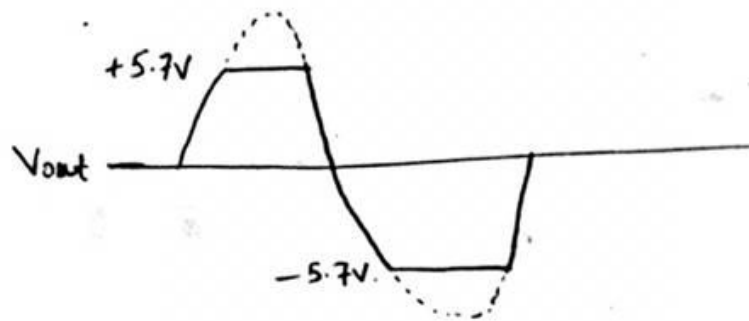Voltage at point A reaches  $-5.7V$ .  
 diode  $D_2$  conducts and limits the -ve waveform.



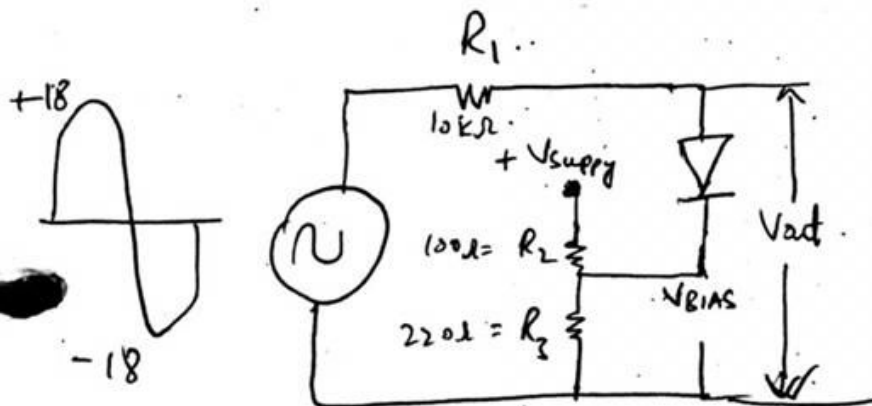Voltage divider bias :- Positive limiter.



$$V_{BIAS} = \left( \frac{R_3}{R_2 + R_3} \right) V_{supply}$$

$$V_{BIAS} = \left( \frac{220}{100 + 220} \right) 12 = 8.25V$$

$$V_{BIAS} = 8.25$$






Diode clippers :-

clippers adds a dc level to an ac voltage.


positive clipper operation :

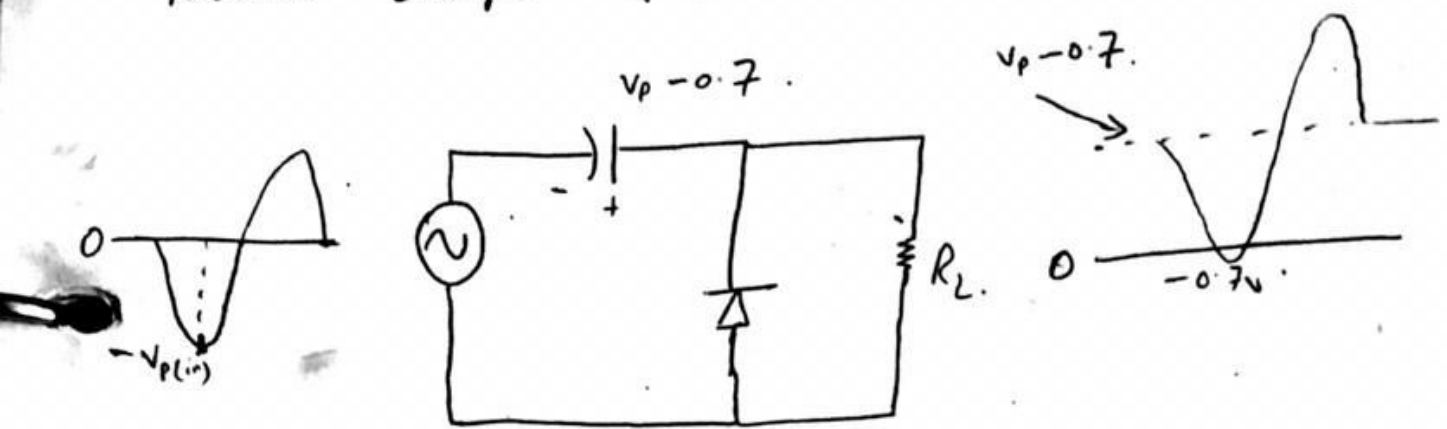

First half of negative peak diode act as F.B and capacitor gets charged.

As second half of <sup>positive</sup> negative peak diode act as R.B and capacitor start discharging. Capacitor become a battery source in series with ac signal and the value of this battery source offset the signal.

Negative clamper operation :-

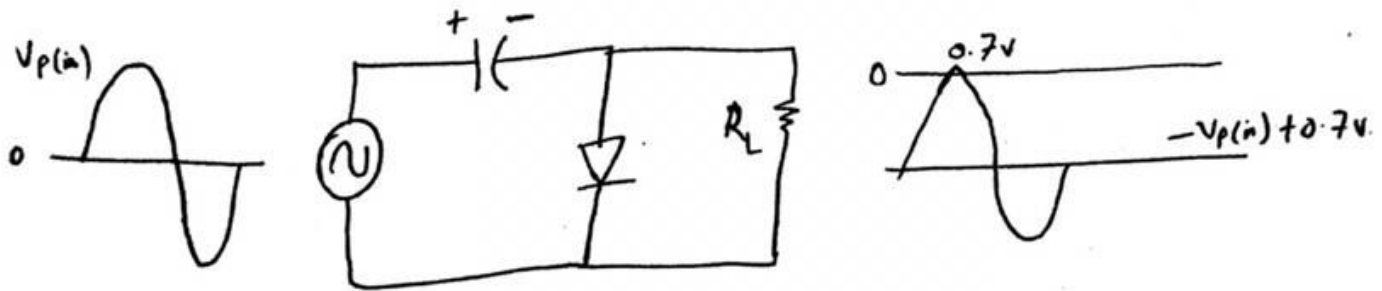

Special purpose diodes :-

Zener diodes, Varactor diodes, optical diodes,