

SEQUENTIAL LOGIC




FLIP FLOP D- FLIP FLOP JK- FLIP FLOP T- FLIP FLOP

DIGITAL LOGIC DESIGN

Iqra Chaudhary (Lecturer CS dept. [NUML](#))

Flip-Flops

★ Controlled latches are level-triggered

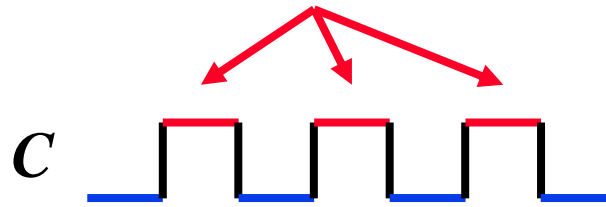


★ Flip-Flops are edge-triggered




D Latch (*D* = *Data*).....(Repeat)

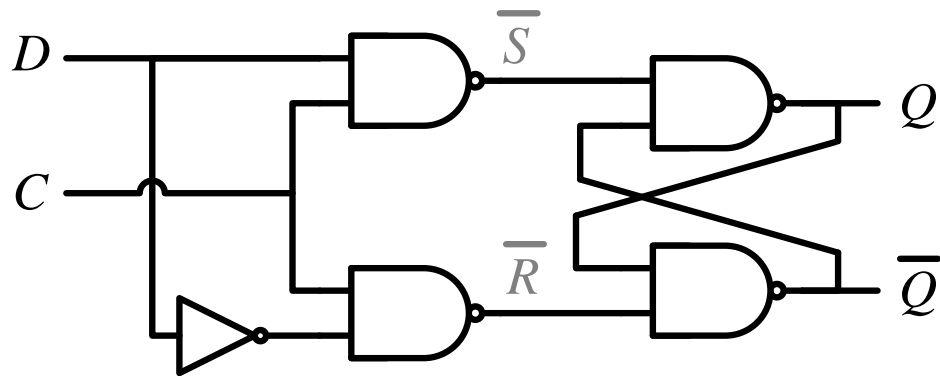★ *Flip flop are constructed by combining two D Latches with a clock signal*



Timing Diagram

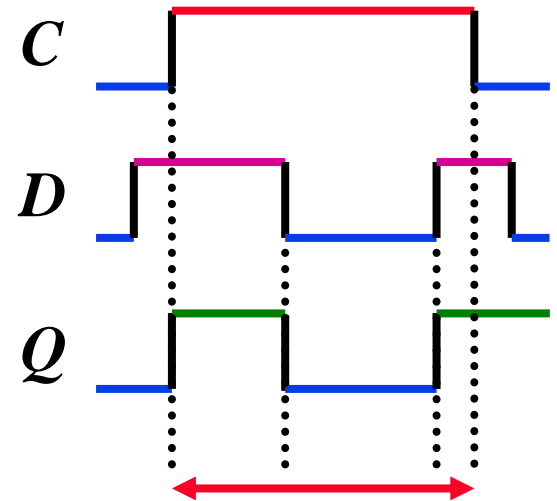

*Output may
change*

<i>C</i>	<i>D</i>	<i>Q</i>
0	x	Q_0
1	0	0
1	1	1


No change

Reset

Set


Flip-Flops

★ Master-Slave *D* Flip-Flop

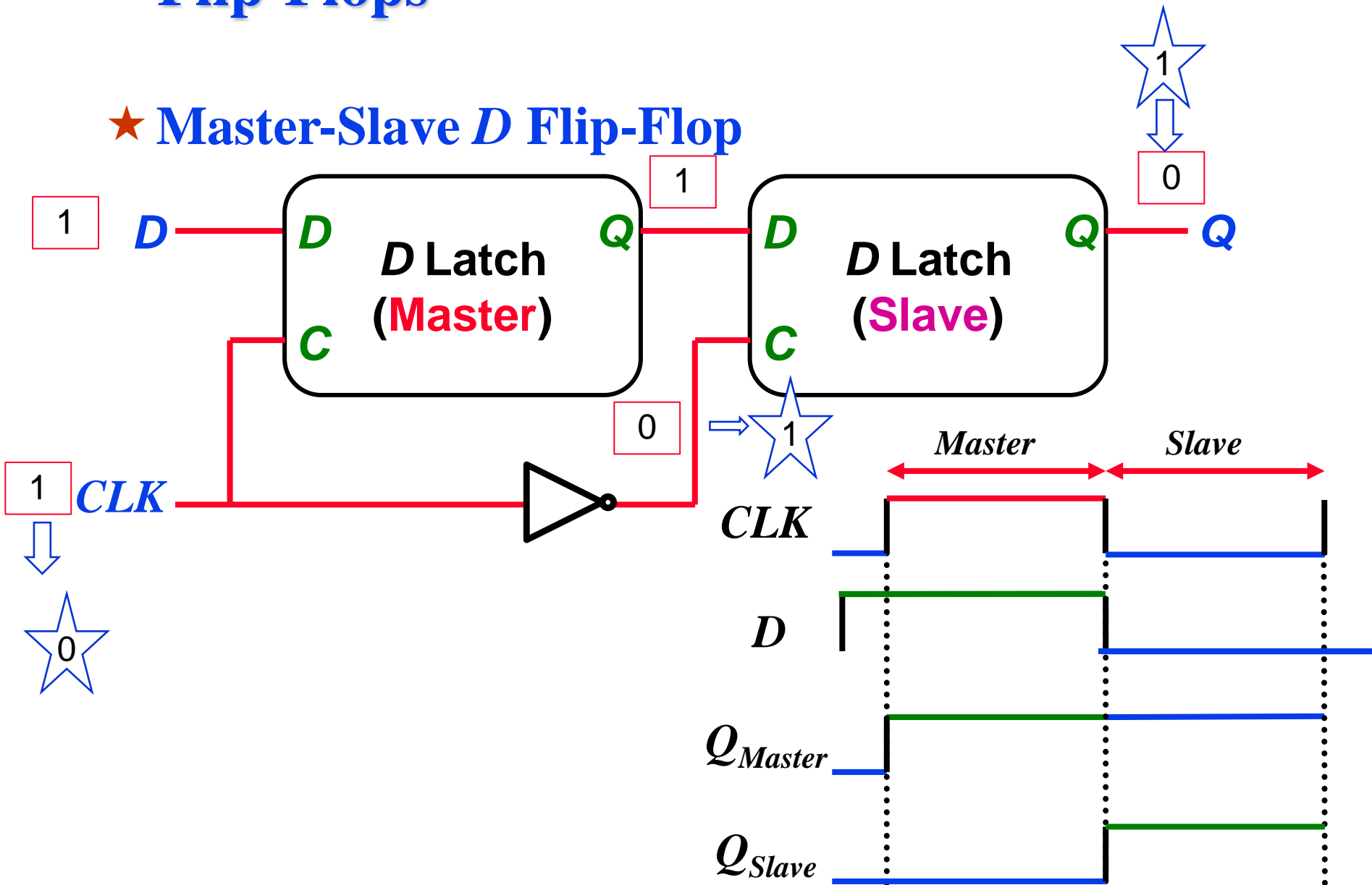


Flip-Flops

★ Master-Slave *D* Flip-Flop

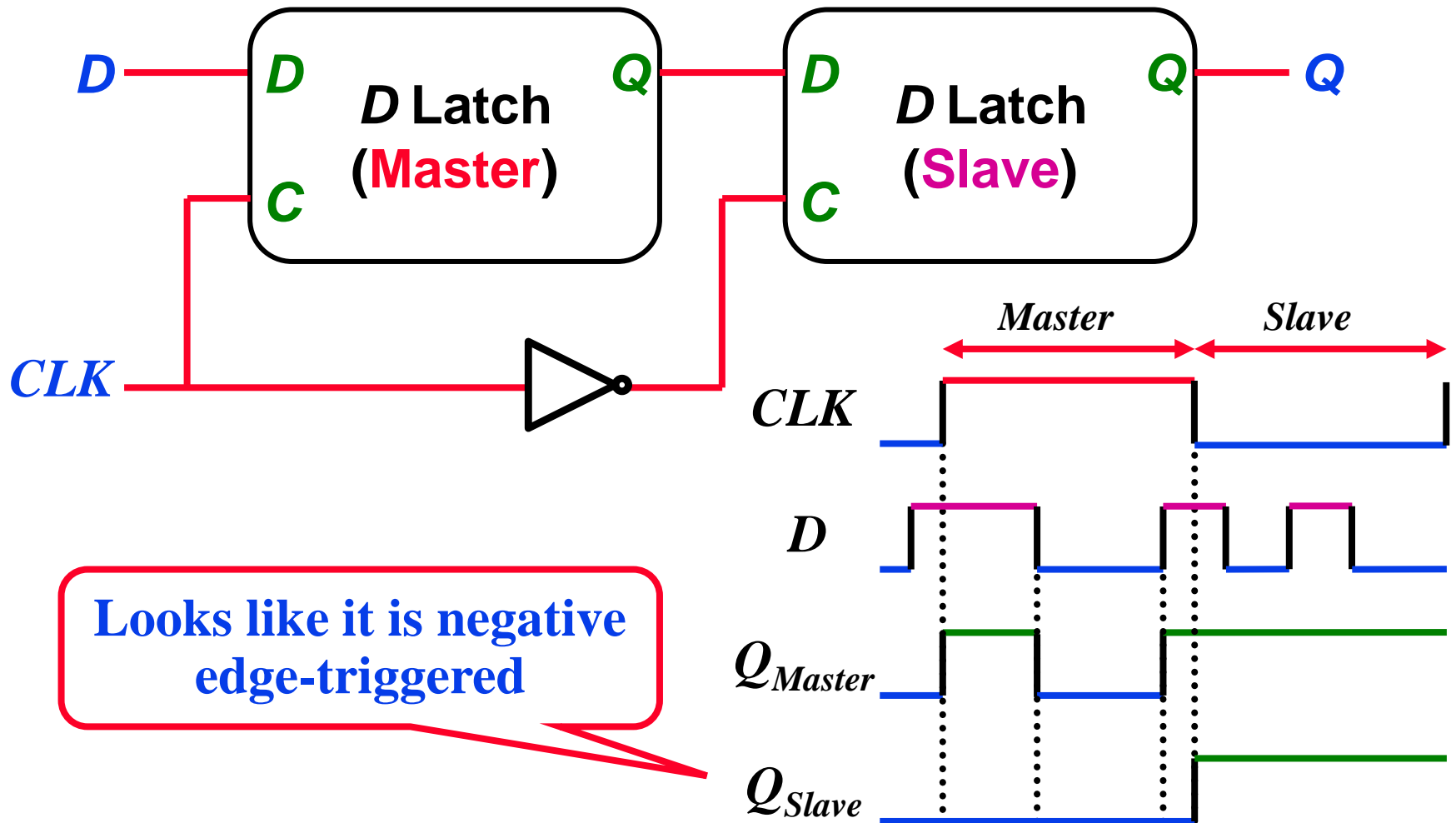


Flip-Flops

★ JK Flip-Flop

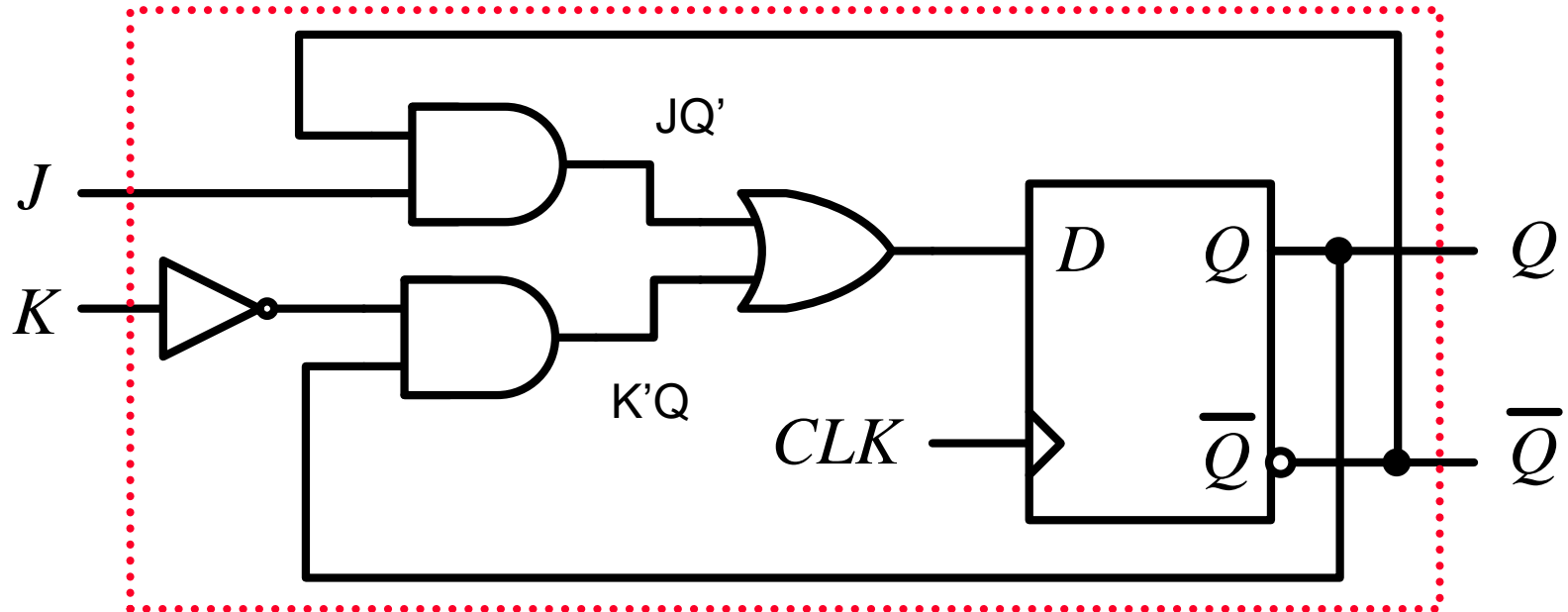



$$D=Q(t+1) = JQ' + K'Q$$

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$Q'(t)$

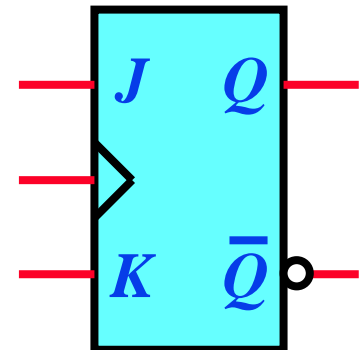

Flip-Flops


★ *T* Flip-Flop

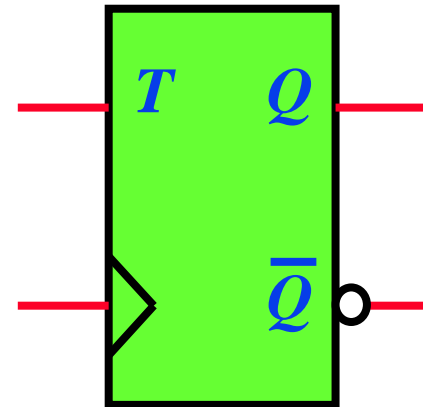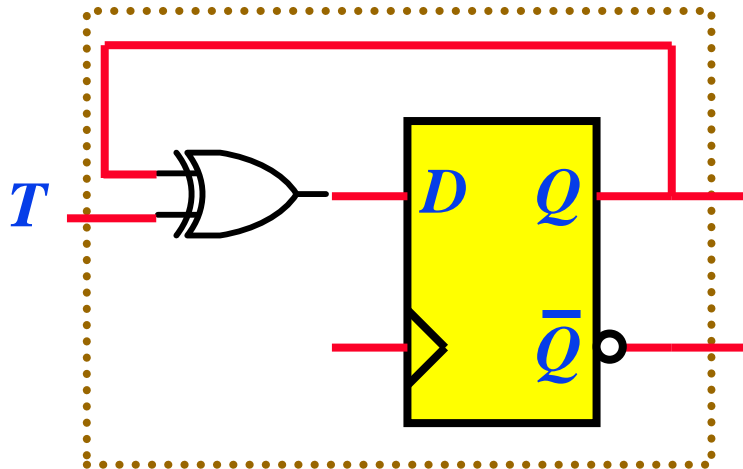

$$D = T \oplus Q$$

T	$Q(t+1)$
0	$Q(t)$
1	$Q'(t)$


Flip-Flop Characteristic Tables

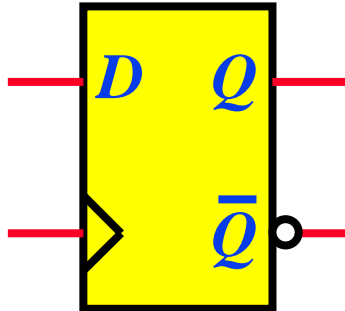

D	$Q(t+1)$
0	0
1	1

Reset

Set

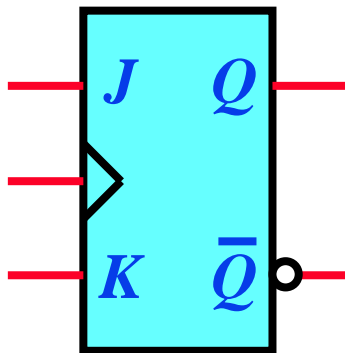


J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$Q'(t)$

No change

Reset

Set

Toggle

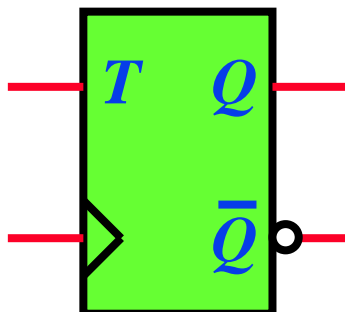


T	$Q(t+1)$
0	$Q(t)$
1	$Q'(t)$

No change


Toggle

Flip-Flop Characteristic Equations

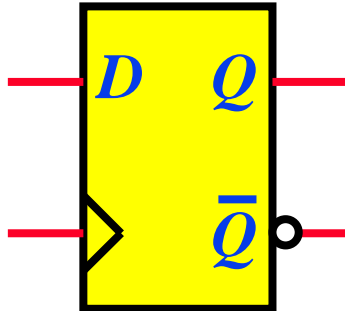


D	$Q(t+1)$
0	0
1	1

$$Q(t+1) = D$$

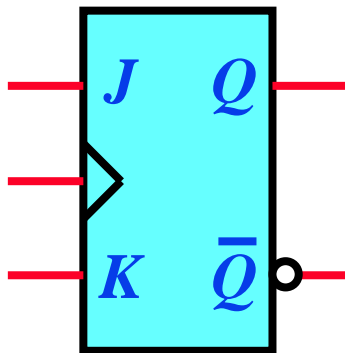

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$Q'(t)$

$$Q(t+1) = JQ' + K'Q$$

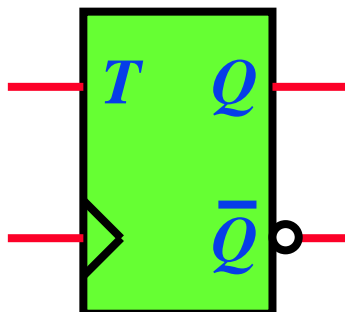

T	$Q(t+1)$
0	$Q(t)$
1	$Q'(t)$

$$Q(t+1) = T \oplus Q$$