

Experiment#3

Title:-

Application of logic gates “Implementation of De Morgan’s law”

Objective:-

- DeMorgan’s law

- $\overline{(A+B)} = \bar{A} \cdot \bar{B}$
- $\overline{(A \cdot B)} = \bar{A} + \bar{B}$

Parts required:-


- IC Type 7408 Quadruple 2-input AND gates
- IC Type 7432 Quadruple 2-input OR gates
- IC Type 7404 Quadruple 1-input NOT gates

Equipment required:-



- Trainer/ proto board
- Wire cutter
- Patch Cord
- Voltmeter

Theory:-


DeMorgan’s law

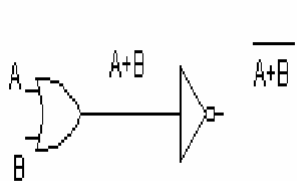

Is equivalent to:

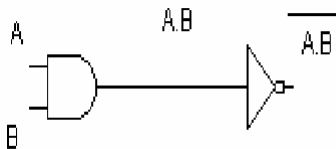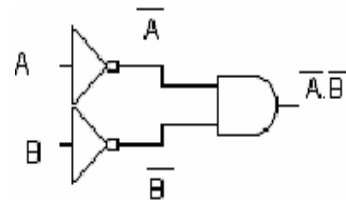

Is equivalent to:

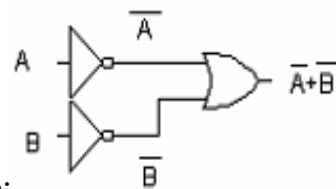

Procedure:-

- (a) Place the IC of required on the bread board. Be sure that it is seated firmly, straddling the notch in the socket, and that none of the pins are bent
- (b) connect $V_{cc}=5V$ to pin 14 and Ground to pin 7
- (c) Pin lay out of the IC is given in Annex connect one of gates. Connect inputs(pin1&2)to SW1 and SW2 and output to the LED
- (d) Switch ON the circuit and complete following truth tables

(e)For DeMorgan's law $\overline{A+B} = \overline{A} \cdot \overline{B}$

A	B	A+B	$\overline{A+B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$

And

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

A	B	A.B	$\overline{A \cdot B}$	\overline{A}	\overline{B}	$\overline{A} + \overline{B}$

Question:- Draw the logic circuit diagrams and describe the connections.